

14

DSO

Md. Ashif Mahmud Joy

011 172 067

Sec: B

Ans. to the Question - No-1

8 Arithmetic operation, 4 logical operation

Ans. to the Question - No-2

expected form of x and y is given below:

<u>Cin</u>	<u>operation</u>	<u>x</u>	<u>y</u>
0	$A + B'$	A	B'
1	$A + B' + 1$	A	B'

Ans. to the Question - No-4

a) If $A = \text{all } 1\text{'s}$

And ~~a~~ $C_{in} = 1$

Then after the arithmetic operation $Count = 1$

b) $F = A - B$

$$= A + \bar{B} + 1$$

$$= A + 2^n - 1 - B + 1 \geq 2^n$$

$$= A - B \geq 2^n$$

Ans. to the Question-No-5

1 register is needed

Ans. to the Question-No-6

Excitation table of JK Flip-Flop is given below:

<u>Outputs</u>		<u>Inputs</u>	
<u>Q_n</u>	<u>Q_{n+1}</u>	<u>J</u>	<u>K</u>
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Ans. to the Question-No-7

Expected combinational Circuit :

For clear : $J-K = 0, 1$

$$JA_i = 0$$



$$KA_i = P_2$$

Ans. to the question-No-8

Current A_i	B_i	B_{0i}	Next A_i	B_{0i+1}	JA_i	KA_i
0	0	0	0	0	0	X
0	0	1	1	1	1	X
0	1	0	1	1	1	X
0	1	1	0	1	0	X
1	0	0	1	0	X	0
1	0	1	0	0	X	1
1	1	0	0	0	X	1
1	1	1	1	1	X	0

A_i	$B_i B_{0i}$ 00	01	11	10
0	0	1	0	1
1	X	X	X	X

$$JA_i = A_i + \overline{B_i} B_{0i} + B_i \overline{B_{0i}}$$